



1) Simplify the following function and then implement it using 2-Level (NOT) Gates only?

a. $E(W, X, Y, Z) = \overline{(0, 2, 4, 5, 8, 9, 10, 14)}$ $\Phi(W, X, Y, Z) = \overline{(1, 6, 13)}$

$F' = yz + wx y' \rightarrow \text{SOP}$


$F = (yz + wx y')$

$F = (y'z') \cdot (w + x + y)$
POS

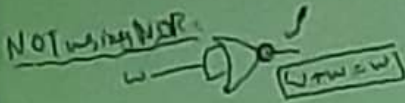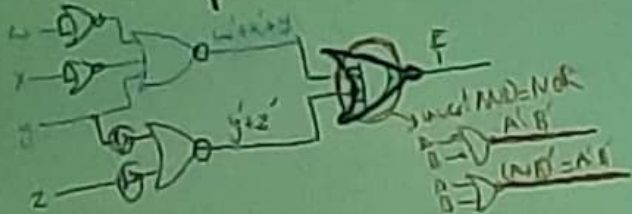

$F' = \text{sum of product}$
K-map
Homogeneous

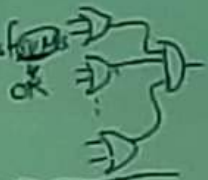$F = \text{product of sum} = (\text{sum of product})'$






3) Simplify the following Function and then implement it using 2 Level (NOR) Gates only?

$$F(W, X, Y, Z) = (0, 2, 4, 5, 8, 9, 10, 14) \quad G(W, X, Y, Z) = (1, 6, 13)$$

$$F' = yz + wx'y' \rightarrow \text{SOP}$$

$$F = (yz + wx'y')$$

$$F = (yz)' = (w' + x' + y')$$

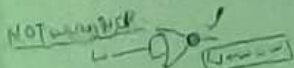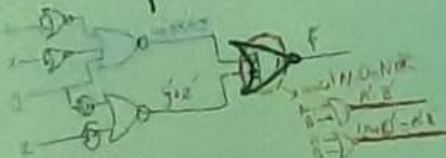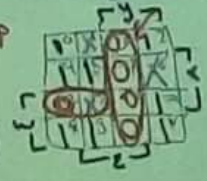


$$F' = \text{sum of product of minterms}$$

$$F = \text{product of sum} = (\text{sum of products})'$$





2) Simplify the following Function and then implement it using 2-Level

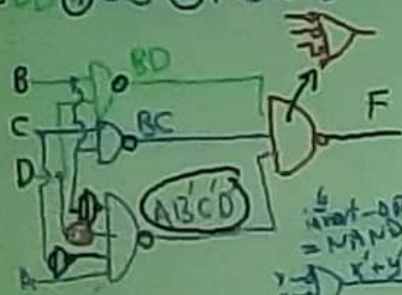a. $F(A, B, C, D) = (5, 6, 7, 8, 13, 14, 15)$
 $F = BD \oplus BC \oplus AB'C'D'$ SOP



1st input - OR
 $x + y = (xy)$
 $x + y = (xy)$

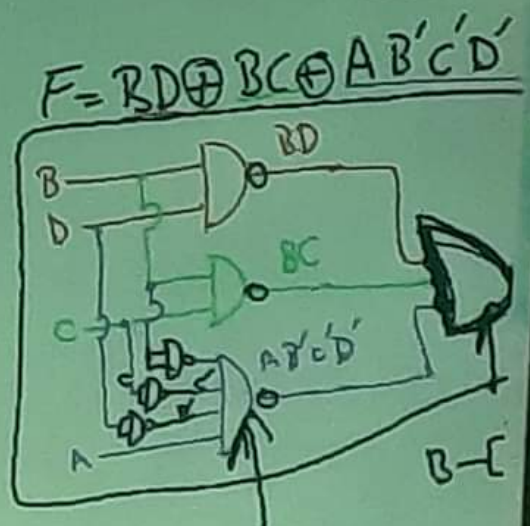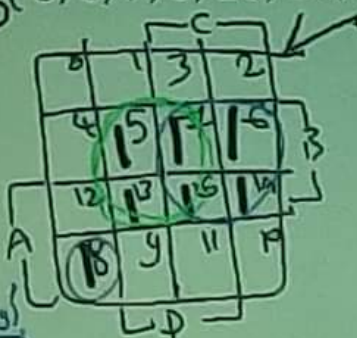implement NOT using NAND: $x \rightarrow x \text{ NAND } x$



Using NOR

input A




input B



input C



input D

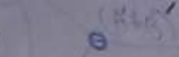

input E



input F




input G




input H



input I

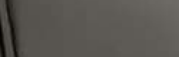

input J

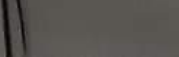

input K



input L



input M



input N



input O



input P



input Q




input R







Logic Diagram


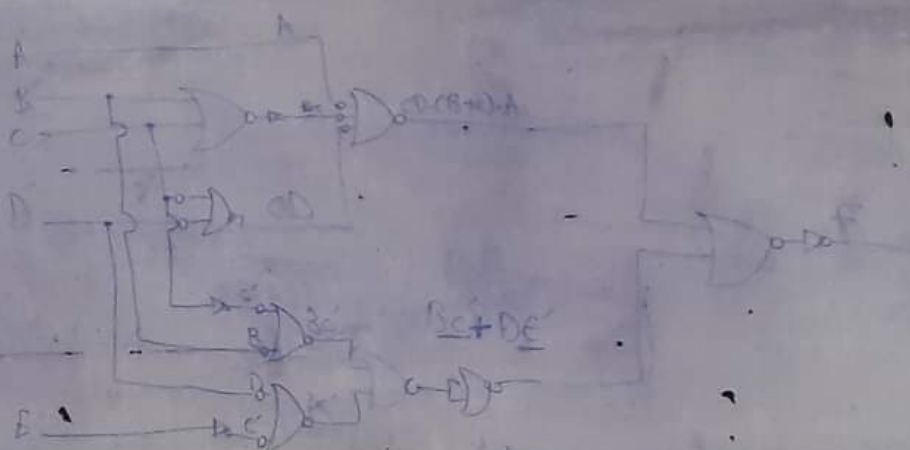
$$F(A, B, C, D) = (C \times B) + (B' + D'E')$$



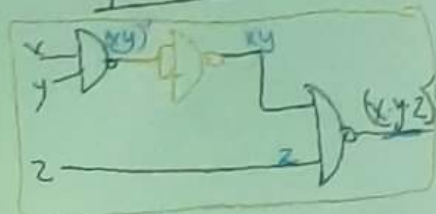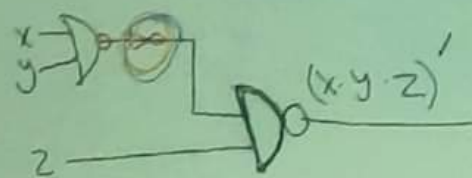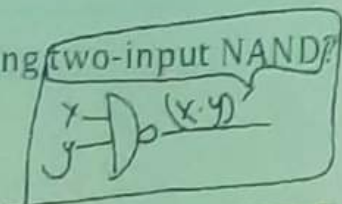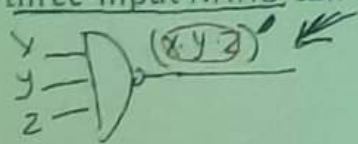1) How the three-input NAND can be expanded using two-input NAND?



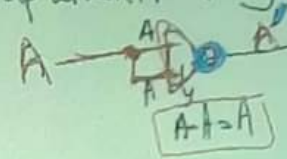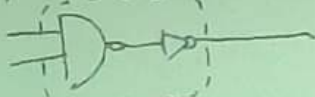
implement AND using NAND { implement NOT using NAND




$$A \cdot A = A$$

Using NOR


implement NOT.

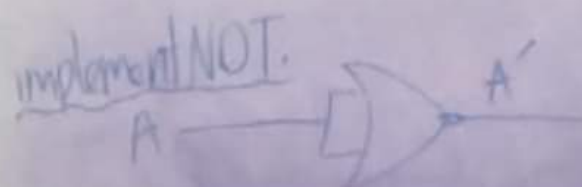

implement OR.

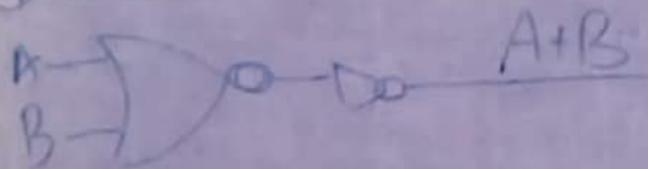


implement AND.

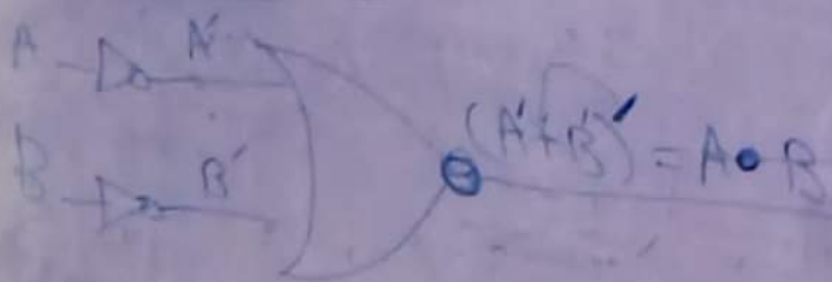


using NAND


implement NOT

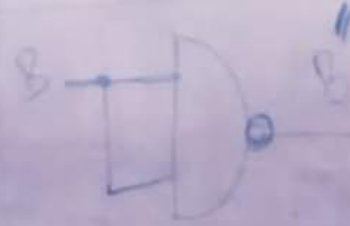

implement AND

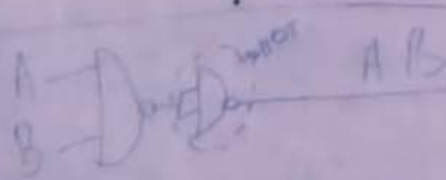


implement OR

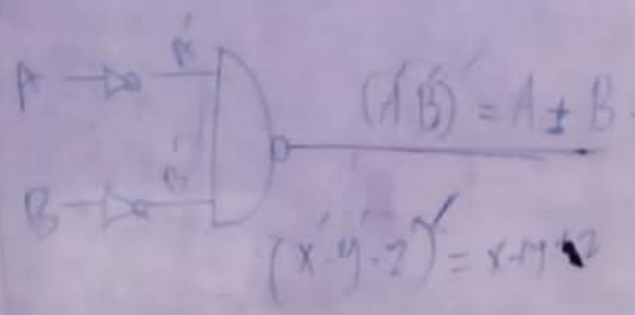

(3) + (w)

w

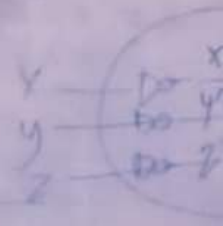

x
 y
 z

Parity checker

step 1 no. of inputs : x y z p


output : ~~F~~ F

step 2 :

X	y	z	p	F false	F false	A $x \oplus y$	B $z \oplus p$	A \oplus B
0	0	0	0	1	0	0	0	1
0	0	0	1	0	1	0	1	0
0	0	1	0	0	0	0	1	0
0	0	1	1	1	1	0	0	1
0	1	0	0	0	0	1	0	0
0	1	0	1	1	1	1	1	1
0	1	1	0	0	0	1	0	0
0	1	1	1	1	1	1	0	0
1	0	0	0	0	0	1	0	0
1	0	0	1	1	1	1	1	1
1	0	1	0	1	0	1	1	1
1	0	1	1	0	1	1	0	0
1	1	0	0	1	0	0	0	1
1	1	0	1	0	1	0	1	0
1	1	1	0	0	1	0	1	0
1	1	1	1	1	0	0	0	1

step 3


$$F = \sum (0, 3, 5, 6, 9, 10, 12, 15)$$

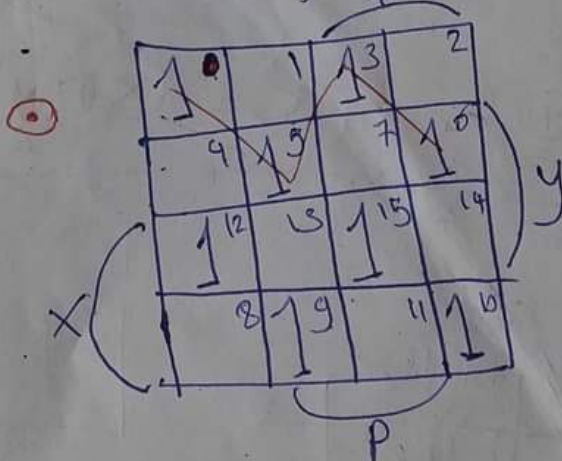

$$F = x \oplus y \oplus z \oplus p$$

$$= (x \oplus y) \oplus (z \oplus p)$$

step 4

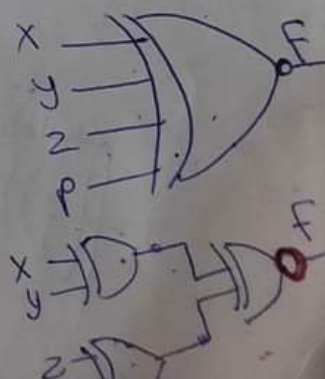

4) Design an odd Parity generator / Parity checker circuits

step 1 Parity generator


3 inputs x, y, z
one output P

step 2 truth table

X	y	z	P	$x \oplus y$
even 0	0	0	1 m_0	0
0	0	1	0 m_1	0
0	1	0	0 m_2	1
even 0	1	1	1 m_3	1
1	0	0	0 m_4	1
even 1	0	1	1 m_5	1
1	1	0	1 m_6	0
1	1	1	0 m_7	0

Note: P72

step 3 $P = \sum (0, 5, 6, 3)$

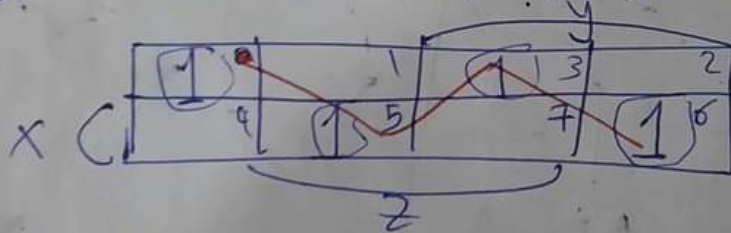


~~$P = x \oplus y \oplus z$~~


$P = x \oplus y \oplus z$

Exclusive NOR
 $= (x \oplus y \oplus z)'$

step 4

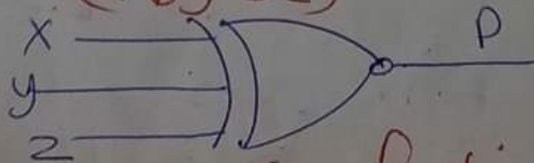

Even function

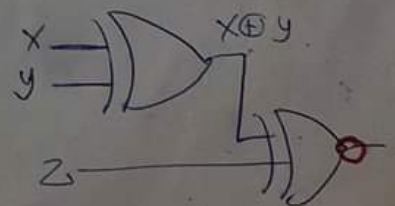

$F6 = xy' + x'y$

$F6 = x \oplus y$

Exclusive-OR
(X or y, but not both)
(odd function)

$F8 = xy + x'y'$

$= (x \oplus y)'$

$= x \odot y$


Equivalence
Exclusive-NOR
(X equals y)
(even function)

Lab 5 (NOR only)

Objective: implementing functions using NOR only.

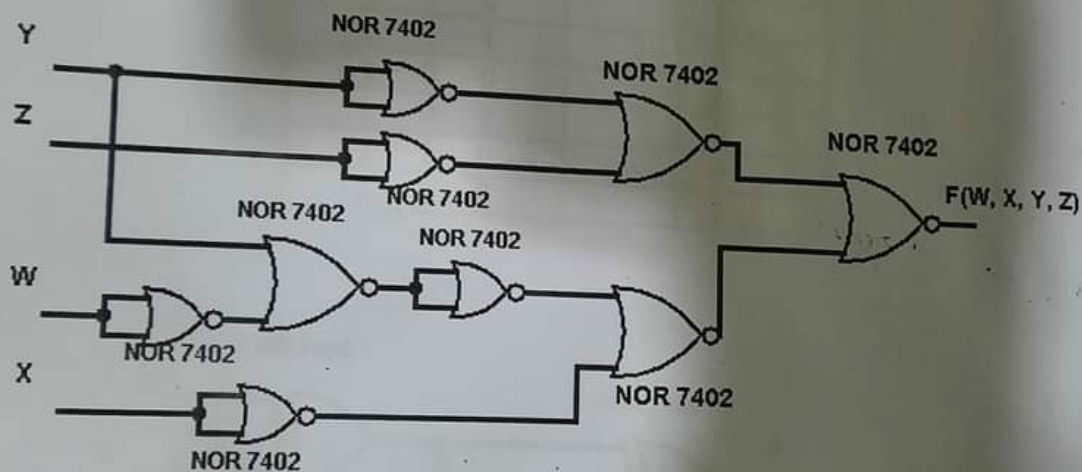Task to do in lab: implementing practically the following function using NOR only.

$$F(W, X, Y, Z) = (Y' + Z')(W' + X' + Y)$$



$$F(W, X, Y, Z) = \sum(0, 1, 2, 4, 5, 6, 8, 9, 10, 14)$$